


## Physics 242 – Electronics

### Experiment 3 – RC Low-Pass Filter

#### Introduction

The complex impedances of the capacitor and inductor depend on frequency. Therefore, AC circuits containing capacitors and inductors can exhibit a frequency-dependence, serving as filters with a frequency-dependent response. Two of the simplest and most useful filter circuits are the RC low-pass and RC high-pass filters, which are in essence frequency-dependent voltage dividers. In this experiment, we will investigate the behavior of single-stage and two-stage RC low-pass filters.


#### Procedure and Questions

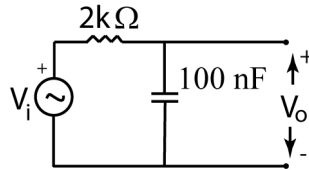

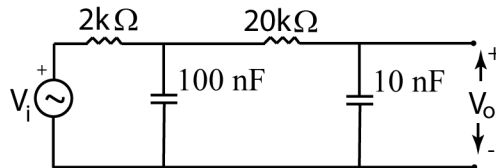1. Construct the circuit shown above, using a nominally  $2\text{ k}\Omega$  resistor and  $100\text{ nF}$  capacitor. Measure your component values first, using the LCR meter to measure the capacitance. Set the amplitude of your function generator to  $1.0\text{ V}$  peak-to-peak. Measure  $V_i$  with the oscilloscope. Then measure the peak-to-peak amplitude  $V_o$  carefully with the 'scope at a series of frequencies from  $1\text{ Hz}$  to  $1\text{ MHz}$ , or whatever is the maximum frequency provided by your signal generator. Since the frequency range spans several orders of magnitude, you'll plot your results on a log scale, so it's most efficient to use frequencies that vary logarithmically, like  $1, 2, 5, 10, 20, 50$ , etc. Take a few extra measurements around the point where the amplitude of  $V_o$  first begins to decrease. Also, calculate the cut-off frequency of the filter (the frequency at which the output voltage is reduced by a factor of  $\sqrt{2}$ ; i.e. where  $V_o = \frac{1}{\sqrt{2}} V_i$ ) and measure the output voltage at the cut-off frequency.

Plot the amplitude ratio in decibels vs. frequency  $f$ . Use a log scale for the frequency axis.

Recall that the amplitude ratio in decibels is given by  $20 \log_{10} \left( \frac{V_o}{V_i} \right)$ . Fit a line to the straight-line part of the plot where the amplitude ratio is decreasing steadily. Is the slope near the predicted value of  $20\text{ dB}$  decrease per decade of frequency?



2. Next, build a second low-pass filter stage to follow your existing filter circuit. Use a resistor of nominal value  $20\text{ k}\Omega$  and a capacitor of nominal value  $10\text{ nF}$  (but measure their actual values

before connecting them into your circuit). For a 1.0 V peak-to-peak input voltage, measure the output voltage as a function of frequency as before (but you need not take extra point around the cut-off frequency this time). Make a plot as before, and measure the slope in the region where is exhibits a linear decrease. What slope value do you find? Is the measured value in accord with your expectations for a two-stage RC low-pass filter? Explain briefly.